



# 6th Ed. Associate CET Study Guide Errata Sheet

An updated version of the Associate CET Study Guide Errata Sheet can be found online at [www.eta-i.org/6thEdASTErrataSheet.pdf](http://www.eta-i.org/6thEdASTErrataSheet.pdf)

## Resonance, Page 23

".0159" should be .159 and the square root sign should not be in the third step of the example:

$$f_r = \frac{.159}{\sqrt{(2 \times 10^{-4}) \times (2 \times 10^{-10})}}$$

$$f_r = \frac{159 \times 10^{-3}}{\sqrt{4 \times 10^{-14}}}$$

$$f_r = \frac{159 \times 10^{-3}}{2 \times 10^{-7}}$$

### A further remark on the solution:

If you remember your order of math operation rules and your common denominator rules, use your calculator strokes as:

Take  $\sqrt{LC}$  as **200 $\mu$ H** times **200pF** (or .0002 times .0000000002 on your calculator). You then keystroke the  $\sqrt{\text{square root}}$  key, resulting in .0000002 (or  $2 \times 10^{-7}$  as you see in the equation).

Then you multiply .0000002 to 2 to the  $\pi$  button on your calculator. This results in .000001256637061 on the screen, your denominator. Then you keystroke the 1/X button resulting in 795,774.7154594766. Recall your answer choices above and the result is 795 kHz.

*Be sure you know your Electronics Units!*

## AC Circuit Operations, Page 47

"13.2K $\Omega$ " should be 132.6K $\Omega$  in the formula below:

$$XC = \frac{1}{6.28 * 30 \times 10^3 * 40 \times 10^{-12}} = 132.6K \Omega$$

## AC Circuit Operations, Page 48

"W" should be an " $\Omega$ " symbol in  $R_1$ ,  $X_{L1}$  and  $X_{C1}$  below:

Source Voltage = 120V  
 Source Frequency = 50 KHz  
 $L_1 = 10\text{mH}$   
 $C_1 = 100\text{pF}$   
 $R_1 = 300\Omega$

### BASED ON THE VALUES GIVEN

$$X_{L1} = 6.28 * (50 \times 10^3) * (10 \times 10^{-3}) = 3.14K\Omega$$

$$X_{C1} = 1 / 6.28 * (50 \times 10^3) * (100 \times 10^{-12}) = 31.8K\Omega$$


$$I_{R1} = V_T / R_1 = 400\text{mA}$$

$$I_{C1} = V_T / X_{C1} = 3.77\text{mA}$$

$$I_{L1} = V_T / X_{L1} = 38.2\text{mA}$$

$$I_T = \sqrt{I_r^2 + I_{XNET}^2} = 401\text{mA}$$
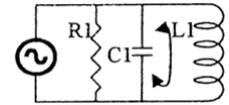
$$I_{XNET} = \text{Difference between the Inductive and Capacitive Currents}$$



$$I_{\text{net}} = I_{C1} - I_{L1}$$

$I_{\text{net}}$  represents only the out-of-phase currents

## Semiconductors, Page 74

"(highest voltage gain)" should be under #2 (not #1) and input should be "output" under #3:

1. **Common emitter** - like the circuit in Fig. 16
2. **Common base** - where the input signal is applied to the emitter rather than the base (highest voltage gain)
3. **Common collector** - has high input impedance (and low output impedance)

## Chapter 9 Quiz, Page 78

#9 - C



# 6th Ed. Associate CET Study Guide Errata Sheet

An updated version of the Associate CET Study Guide Errata Sheet can be found online at [www.eta-i.org/6thEdASTerrataSheet.pdf](http://www.eta-i.org/6thEdASTerrataSheet.pdf)

## Chapter 8 Electronic Components, Page 68

The middle paragraph on the right side ("Thermacouple: A thermocouple is a junction...") Thermacouple should be Thermocouple.

## Unit 5 Review Questions, Page 102

The Formulas for C. and D. on question #6, should be:

c.  $1 + \left( \frac{R_f}{R_i} \right)$

d.  $1 - \left( \frac{R_f}{R_i} \right)$

"c" is still correct.

## Chapter 16 Flip-Flops: Sequential logic gates, Page 138

*"S=0" should be "R=0" and the gates are NOR not NAND under the R-S Flip Flop diagram.*

What input state on S will cause Q output to be high? The answer is: When R=0, then S=1, Q=1. You can prove this to yourself by looking back at NOR gate truth table to see that if any input is 1, the output for that NOR is 0.

## Practice Exam #2, Page 202

The answer for Question #2 should be "a. Cache". Cache is internal, whereas Tape Drive (b.) is external memory.

and

The answer for Question #24 should be "d. 2.9 Ohms". The question asks for RESISTANCE, whose units are Ohms, but the correct calculation to use is  $R = E^2 / P$ . You are given the Volts (E or V) and are given the Power (P or Watts) to find Resistance. "d. 2.9 Ohms" is correct  $\Rightarrow 144 / 50 = 2.88$ .

## Common Formulas Sheet, Page 224

*"Inductors connected in series" and "Inductors connected in parallel" are switched:*

Inductors connected in series

$$L = L_1 + L_2 + L_3 + \dots$$

Inductors connected in parallel

$$1 \div L = (1 \div L_1) + (1 \div L_2) + (1 \div L_3) \dots$$